

Experiment-1

Light Emitting Diode and Photodiode Characterizations

Simulation Exercise

1. Write ngspice netlist to measure I/V characteristics of RED, GREEN and BLUE

2. The NGSpice models of the LEDs are as follows:

```
.model red D(Vj=.75 Cjo=175p Rs=.25 Eg=3.2 M=.5516 Nbv=1.6989 N=2.4 Bv=1.7 Fc=.5 Ikf=0  
Ibv=20.245m Is=880.5E-18 Xti=3)
```

```
.model green D(Is=1e-19 Rs=1.5 N=1.5 Cjo=50p Iave=30m Vpk=5)
```

```
.model blue D(IS=93.1P RS=42M N=7.47 BV=5 IBV=30U CJO=2.97P VJ=.75 M=.333 TT=4.32U)
```

3. Run the simulation and plot all the characteristics on the same plot. Call this Plot 1.

4. Now plot a graph of $\ln I_D$ v/s V_D for all the diodes. Call this Plot 2. The slope of the graph is given by

$$\frac{\ln I_{D2} - \ln I_{D1}}{V_{D2} - V_{D1}} = \frac{1}{\eta V_T} \quad (1)$$

Calculate the ideality factor η of each diode from the slope. Also calculate the saturation current I_S from the y-intercept.

5. Calculate the bandgap E_g for each LED using the emission wavelengths as:

$$E_g = \frac{1240}{\lambda} \quad (2)$$

6. From Plot 1, choose a constant value of I_D , say 1 mA. For each diode, find out the value of V_D corresponding to $I_D = 1$ mA.

7. Now plot a graph of V_D v/s E_g for all the diodes. For the chosen value of I_D , you should get one point (V_D , E_g) on the graph for each diode and hence you can plot all five points (for the different diodes) on a single graph.

Hardware Exercise Objectives:


1. To identify that the band gap of LEDs
2. To determine the bandwidth a given LED

Equipment/Components Required:

1. LEDs – Red, Green, Blue,
2. Resistor – 1k Ω
3. Variable power supply
4. Multimeters – one ammeter and a voltmeter

Steps:

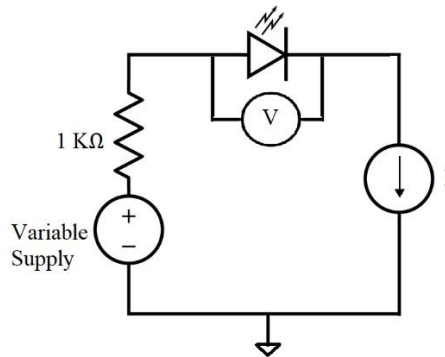1. Make the circuit connections as shown in Figure 1.



2. Vary the supply voltage from 0 – 5V in steps of 0.2 V and measure the V_D and I_D .
3. Tabulate your observations and plot I_D Vs V_D . Name this plot 3.
4. Now plot a graph of $\log I_D$ Vs V_D . Call this plot as plot 4. Calculate the ideality factor η from the slope and the saturation current I_s from the y - intercept for the given diode.
5. Repeat steps 2 to 4 for all the three LEDs.
6. Are the hardware observations same as simulation results?
7. Plot the cut-off voltage Vs E_g for all the five diodes.
8. Calculate the reverse saturation current of each LED using equation given below:

$$I_D = I_{00} e^{-\frac{E_g}{kT}} \left(e^{\frac{qV_D}{kT}} - 1 \right)$$

9. No connect one of the LEDs in series with 1 k Ω resistor and power the LED using a square wave signal of frequency 1 Hz. Set the amplitude of the square wave a little higher than the cut-off voltage of the LED. The voltmeter and the ammeter need not be connected for this circuit. What do you see?

