

## DEVICES AND CIRCUITS LAB REPORT – 3

**EXPERIMENT NAME** : BJT Common Emitter Amplifier Characteristics

**ROLL NUMBERS** : 200020010 , 200020051

**Ng Spice Code** :

\*bjt

vin 1 0 12

R1 1 2 36k

R2 2 0 10k

Rc 1 6 5k

vdc 6 3

Re 5 7 1.99k

vde 7 0

vdb 2 4

Q1 3 4 5 Q2N2222A

.model Q2N2222A NPN(IS=8.11E-14 BF=205 VAF=113 IKF=0.5 ISE=1.06E-11 NE=2 BR=4 VAR=24  
IKR=0.225 RB=1.37 RE=0.343 RC=0.137 CJE=2.95E-11 TF=3.97E-10 CJC=1.52E-11 TR=8.5E-8 XTB=1.5)

.dc vin 0 12 12

\* Control Statements

.control

run

\*white background

set color0=white

\* black grid and text (only needed with X11, automatic with MS Win)

set color1=black

\* wider grid and plot lines

set xbrushwidth=2

print v(3,5) v(5) i(vdc) i(vde) i(vdb)

.endc

.end

No. of Data Rows : 2				
*bjt DC transfer characteristic Wed Dec 29 18:51:52 2021				
Index	v-sweep	v(3,5)	v(5)	i(vdc)
0	0.000000e+00	-9.50284e-25	9.560875e-25	-1.16064e-30
1	1.200000e+01	5.137738e+00	1.962002e+00	9.800520e-04
*bjt DC transfer characteristic Wed Dec 29 18:51:52 2021				
Index	v-sweep	i(vde)	i(vdb)	
0	0.000000e+00	4.804460e-28	4.816066e-28	
1	1.200000e+01	9.859306e-04	5.878563e-06	

By taking  $R_1=36\text{kohm}$ ,  $R_c=5\text{kohm}$ ,  $R_e=2\text{kohm}$  then the values of  $V_e=2\text{v}$ ,  $V_{ce}=5\text{v}$ ,  $I_c=1\text{mA}$ ,  $I_e=1\text{mA}$ ,  $I_b=0.005\text{mA}$  (these values are from calculations)

\*bjt

vin 8 0 dc=0 ac=100m

vcc 1 0 12

R1 1 2 36k

R2 2 0 10k

Rc 1 6 5k

vdc 6 3

Re 5 7 1.99k

vde 7 0

vdb 2 4

Q1 3 4 5 Q2N2222A

cb 2 8 2.040u

cc 6 9 4.080u

RI 9 0 1k

ce 5 0 8u

.model Q2N2222A NPN(IS=8.11E-14 BF=205 VAF=113 IKF=0.5 ISE=1.06E-11 NE=2 BR=4 VAR=24  
IKR=0.225 RB=1.37 RE=0.343 RC=0.137 CJE=2.95E-11 TF=3.97E-10 CJC=1.52E-11 TR=8.5E-8 XTB=1.5)

.ac dec 1000 100 100G

\* Control Statements

.control

run

\*white background

```
set color0=white
```

```
* black grid and text (only needed with X11, automatic with MS Win)
```

```
set color1=black
```

```
* wider grid and plot lines
```


```
set xbrushwidth=2
```

```
plot vdb(9)-vdb(8) xlog
```

```
.endc
```

```
.end
```

ac2: \*bjt

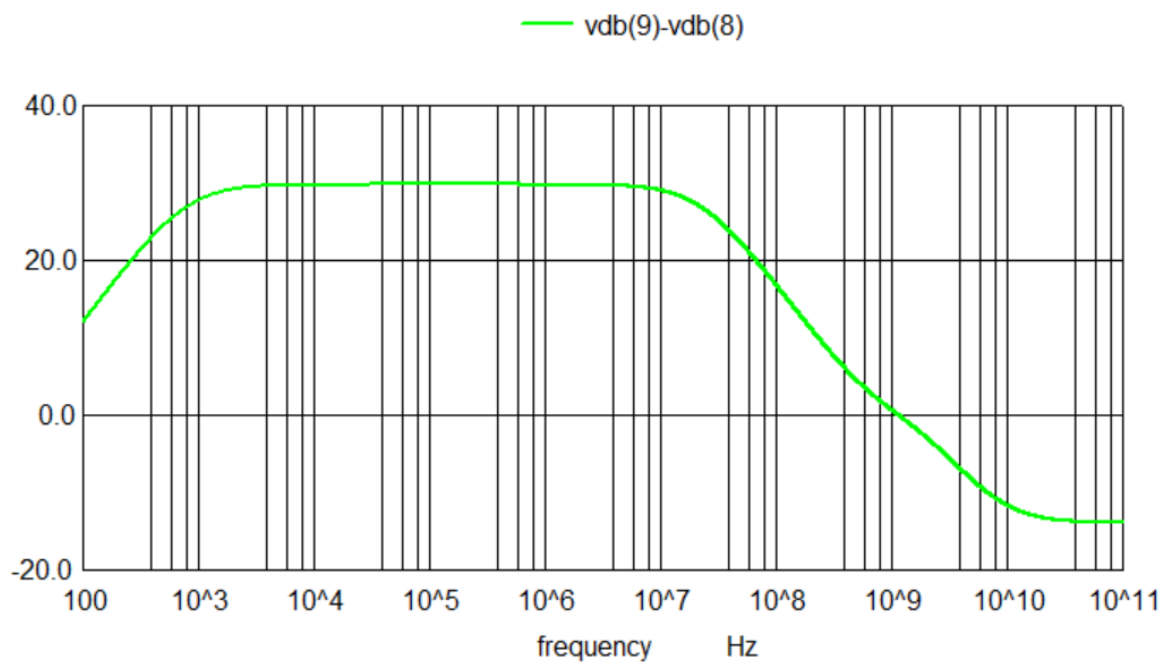

Now here the frequency 2kHz is in mid band region by using  $C_c=4.08 \mu F$  ,  $C_b=2.04 \mu F$  ,  $C_e=8 \mu F$

```
*bjt
```

```
vin 8 0 Sin(0 100m 2k 0 0 0)
```

```
vcc 1 0 12
```

```
R1 1 2 36k
```

```
R2 2 0 10k
```

```
Rc 1 6 5k
```


```
vdc 6 3
```

```
Re 5 7 1.99k
```

```
vde 7 0
vdb 2 4
Q1 3 4 5 Q2N2222A
cb 2 8 2.040u
cc 6 9 4.080u
RI 9 0 1k
ce 5 0 8u
.model Q2N2222A NPN(IS=8.11E-14 BF=205 VAF=113 IKF=0.5 ISE=1.06E-11 NE=2 BR=4 VAR=24
IKR=0.225 RB=1.37 RE=0.343 RC=0.137 CJE=2.95E-11 TF=3.97E-10 CJC=1.52E-11 TR=8.5E-8 XTB=1.5)
.tran 0.1ms 1ms
* Control Statements
.control
run
*white background
set color0=white
* black grid and text (only needed with X11, automatic with MS Win)
set color1=black
* wider grid and plot lines
set xbrushwidth=2


plot v(8) v(9)

.endc
.end
```

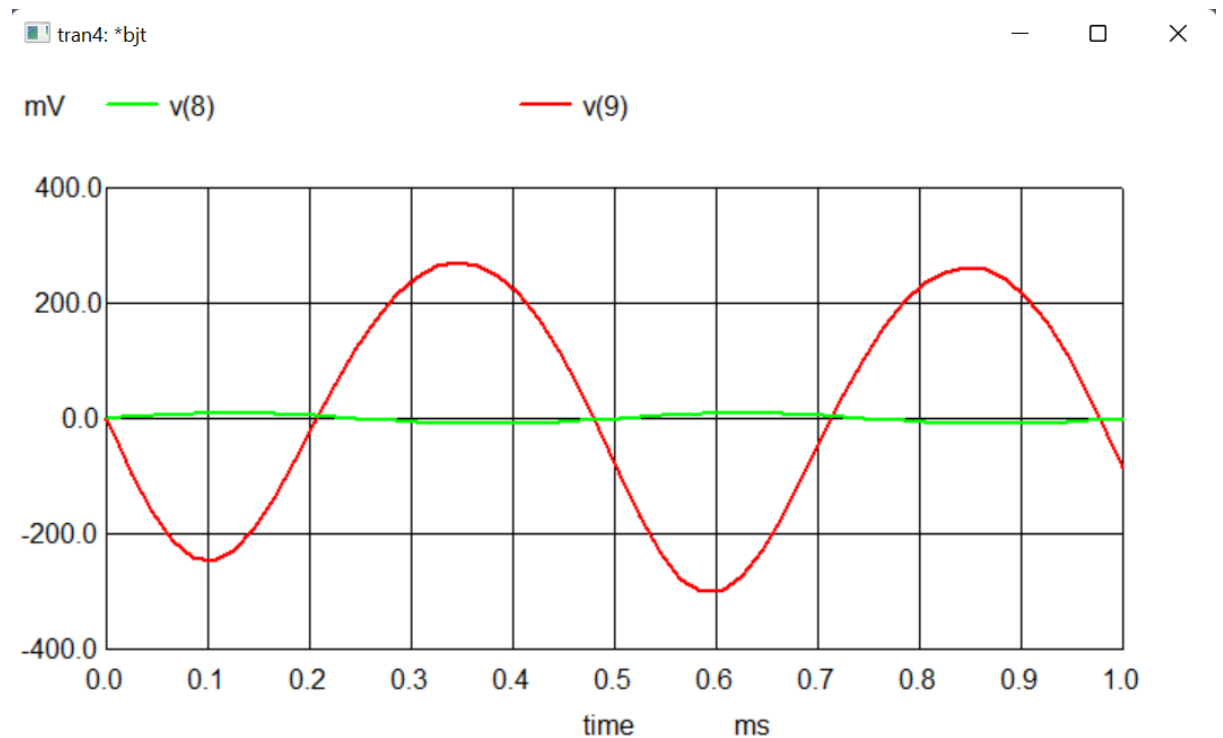


output voltage waveform and input voltage waveform for  $V_{in} = 100 \text{ mVp-p}$  at 2 kHz.

### Observations :

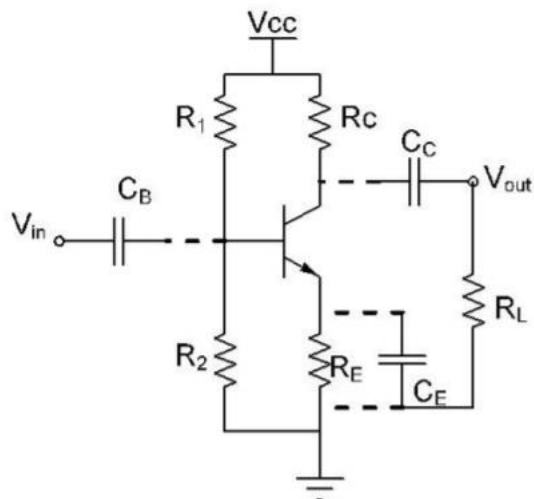


1. We have made the hardware setup as shown in the above figure
2. We observed that we got the output shown in oscilloscope is nearly same like which we got in simulation
3. When we varied frequencies from 100hz to 1.5Meg Hz we got different gains for different frequencies and the data is given below

Frequencies (in Hz)	Input voltage (in V)	Output voltage(in V)	Gain
100	0.36	5	13.88888889
500	0.36	8.6	23.88888889
1000	0.36	10.7	29.72222222
2000	0.36	11.3	31.38888889
3000	0.36	11.5	31.94444444
10000	0.36	11.3	31.38888889
30000	0.36	11.3	31.38888889
70000	0.36	11.1	30.83333333
100000	0.36	11.1	30.83333333
200000	0.36	10.9	30.27777778
250000	0.36	10.7	29.72222222
350000	0.36	10.5	29.16666667
450000	0.36	9.8	27.22222222
600000	0.36	9	25
800000	0.36	8.4	23.33333333
1000000	0.36	8.2	22.77777778
1100000	0.36	7.6	21.11111111
1300000	0.36	7.2	20
1400000	0.36	6.8	18.88888889
1500000	0.36	6	16.66666667

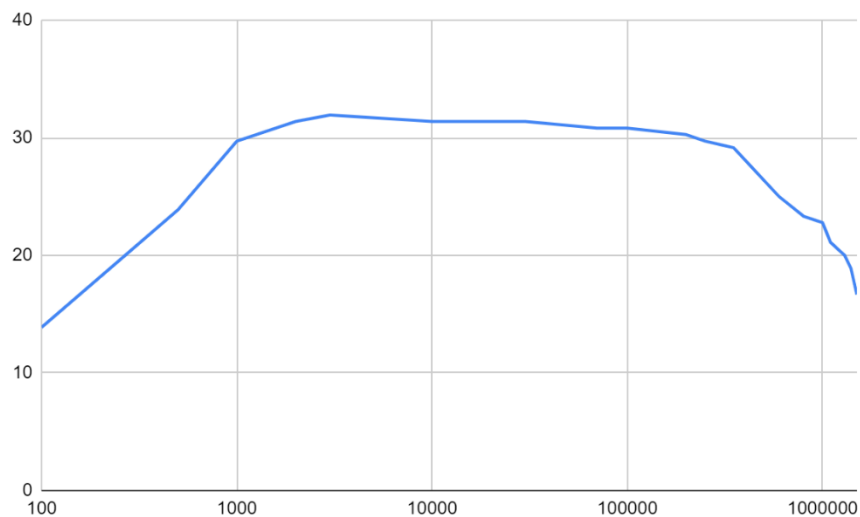


Graph: gain vs frequency

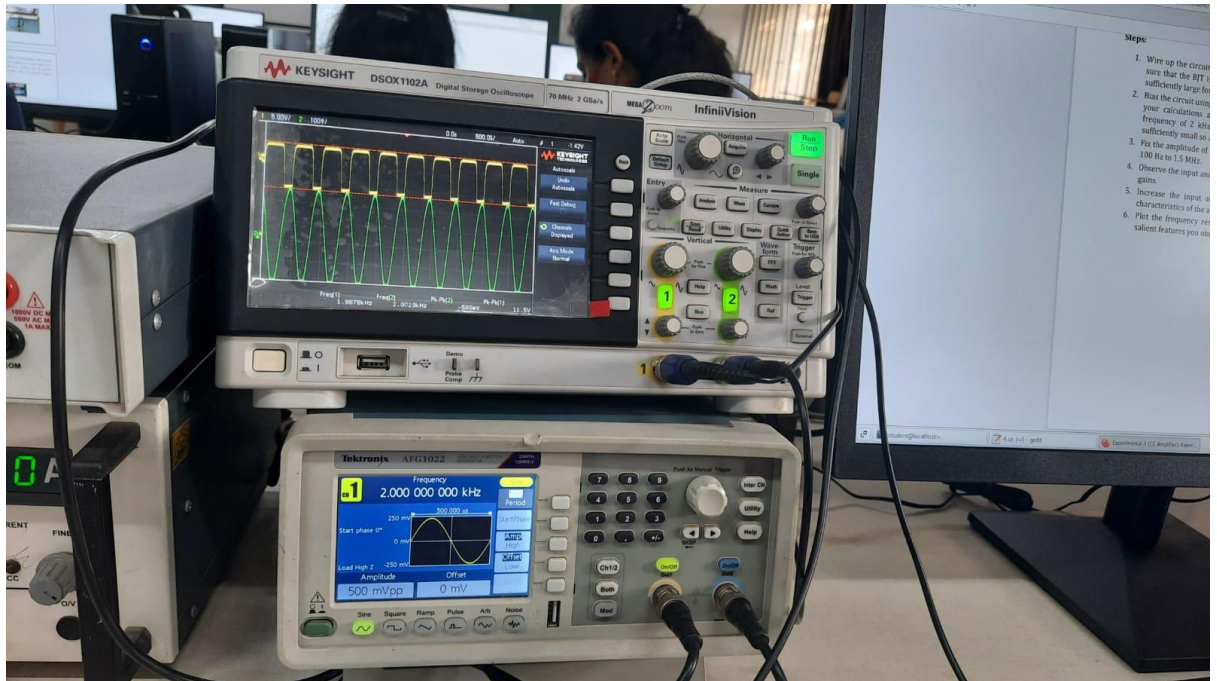- When we increased the input voltage to 500 mVp-p and 1 Vp-p then the clipping will happen to the output signal because the bjt will go to saturation after certain voltage that leads to clipping



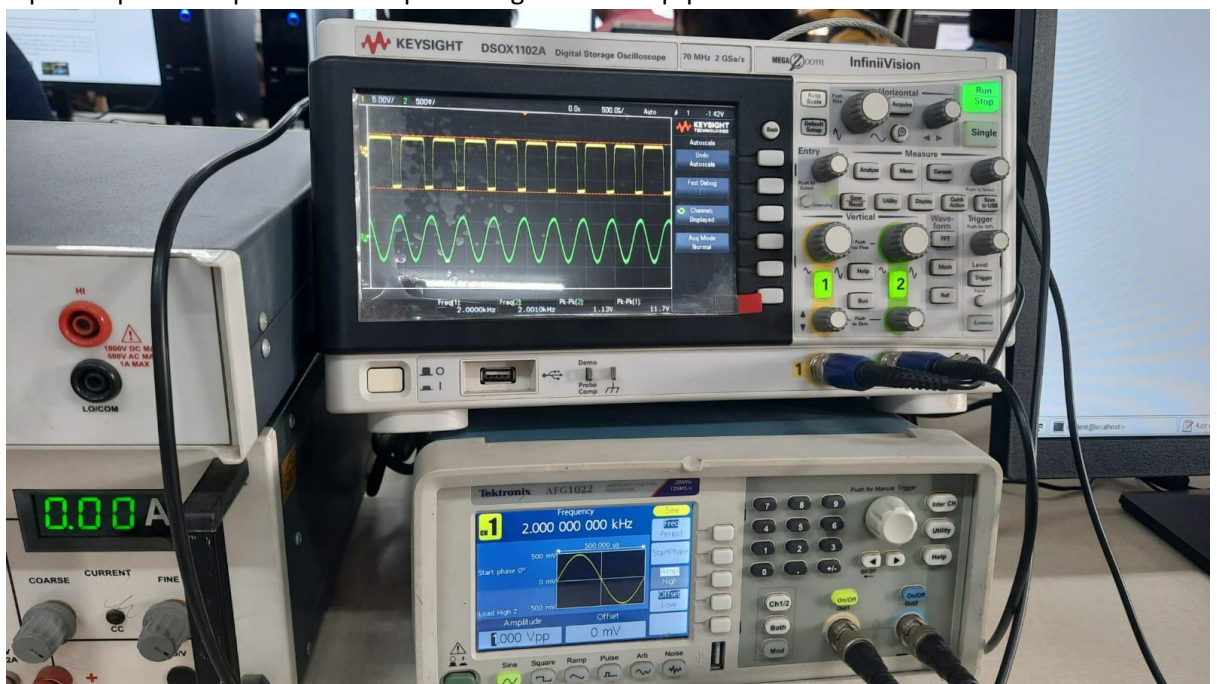Input output of amplifier when input voltage is 500 mVp-p



Input output of amplifier when input voltage is 1 Vp-p

The frequency response plot depicts that upto some frequency the gain is increasing and in the mid region the gain is constant and then again it starts decreasing as increase in frequency

## **Discussion :**

### **200020051:**

In lab 3 we did simulation of BJT model to understand common emitter amplifier properties and we used the oscilloscope and AFG for the first time and we did it well and the oscilloscope helped to see the signals clearly and to understand signals clearly and we did frequency response of BJT amplifier and we came to know about the gain at different frequencies

In this lab there are no issues as such ,but try to give the simulation exercise same as the lab exercise which it will help a lot to cross check the lab results with the simulation results

### **200020010:**

Today in lab 3 we have done simulation and hardware exercise of BJT Common Emitter Amplifier. This lab helped me in understanding the behaviour and characteristics of BJT. We understood about its frequency response and its gain and also about mid-band region.

In hardware exercise we understood how to connect bjt with loads and power supply and with the help of oscilloscope , DSO we could compare the results we got in simulation with that of hardware results.

In third lab we were improved compared to first lab and we need to improve our speed in simulation in future labs.